

Behavioral Verilog modeling at register-transfer level (RTL)

Christian Krieg

October 22, 2024

Welcome to this year's *Digital Integrated Circuits* course! Throughout this course, we will have to solve some assignments that will teach us fundamental concepts of integrated circuit design.

We will demonstrate digital integrated circuit design on a step-by-step simple example of a digital counter. As the name of this course suggests, our ultimate goal is to implement this counter as a digital integrated circuit. In the lab, we map this counter to a [field-programmable gate array \(FPGA\)](#) architecture, and run it on the board shown in Figure 1. The counter's functionality is executed on the [FPGA](#). We will be able to control execution by pushing the buttons, and to visualize the counter value using the [light-emitting diodes \(LEDs\)](#). Because operating a hardware counter with buttons and [LEDs](#) may be inconvenient, we also will interface the hardware counter over a [universal asynchronous receiver/transmitter \(UART\)](#), so that we may be able to further process the counter value on a host computer. But this will all happen during the lab week at the end of the exercises.

 


Figure 1: The *icebreaker* board, which will run our counter

Before we can bring our counter on hardware, it is important that we learn how to design digital circuits using state-of-the-art (and beyond) methods and tools, and to get a feeling for the results of our design decisions. We will draw attention on the results of the synthesis steps, which we will verify with several tools along the digital design flow.

Generally speaking, we perform the following steps:

1. Specify the counter's behavior
2. **Model (implement) the counter in a [hardware description language \(HDL\)](#)**
3. **Verify the counter's implementation**
4. Synthesize and optimize the counter's [HDL](#) model + verify
5. Map the counter to the target ([FPGA](#)) technology + verify
6. Generate an [FPGA](#) bitstream + verify
7. Configure the [FPGA](#) with the bitstream + verify
8. Run the counter on hardware

Our overall task is to build a synchronous counter that runs in two modes, based on a *mode* switch. The two modes are called *up* and *down*. In *up* mode, the counter increments the counter value by **5** at the rising edge of the clock signal, and in *down* mode, it decrements the counter value by **9** at the rising edge of the clock signal. The counter should implement synchronous reset behavior, such that it is set to an initial value of **-50** upon reset. The counter should never exceed a value of **235**, and should never go below a value of **-230** (the counter value sticks near the minimum/maximum value, until the counting direction changes). The counter value should never be **-11** (the counter should jump over this value by one increment/decrement).

Wrapping up formal verification

In the previous tasks, we learned the basics of simulation (including testbenches), and formal verification. We learned that simulating a [design under test \(DUT\)](#) using a testbench may be more intuitive at the first glimpse, while at the second glimpse, formal verification comes with the huge benefit that we do not have to care about input signals – a model checker cares about them for us. In case we did not come up with a working solution for the previous task, we provide one in Listing 1.

Listing 1: A complete set of assertions that verify the properties of our counter (*tb_counter.sv*)

```
1 module tb_counter (
2     input clk,
3     input rst,
4     input mode,
5     output signed[9:0] cnt
6 );
7     // Instantiate DUT
8     counter dut(
9         .clk(clk),
10        .rst(rst),
11        .mode(mode),
12        .cnt(cnt)
13    );
14    // Connect DUT with assertions
15    bind dut assertions tb (.*);
16 endmodule
17
18 module assertions (
19     input clk,
20     input rst,
21     input mode,
22     input signed[9:0] cnt
23 );
24 // Generate reset sequence
25 reg init = 1;
26 always @(posedge clk) begin
27     if (init) assume(rst);
28     else assume(!rst);
29     init <= 0;
30 end
31 // Check properties
32 always @(posedge clk) begin
33     if (rst) begin
34         assert (cnt == -50);
35     end
36     if (!rst) begin
37         //
38         // Check if counter value is never lower than MIN, larger than MAX, or
39         // equal to INV
40         //
41         assert (cnt <= 235);
42         assert (cnt >= -230);
43         assert (cnt != -11);
44         //
45         // Check if the counter value is correctly incremented and decremented
46         //
47         // Counting up
48         if ($past(mode)) begin
49             if (!$past(rst)) begin
50                 if ($past(cnt) == (-11-5)) // INV - INC, counter jumped over INV
51                     assert ((cnt - $past(cnt)) == (5+5));
52                 else if ($past(cnt) <= 235 && $past(cnt) > (235-5)) // cnt was near MAX
53                     assert ((cnt - $past(cnt)) == 0);
54                 else
55                     assert ((cnt - $past(cnt)) == 5);
56             end
57         end
58         // Counting down
59         if (!$past(mode)) begin
60             if (!$past(rst)) begin
61                 if ($past(cnt) == (-11+9)) // INV + DEC, counter jumped over INV
62                     assert ((($past(cnt) - cnt) == (9+9)));
63                 else if ($past(cnt) >= -230 && $past(cnt) < (-230+9)) // cnt was near MIN
64                     assert ((($past(cnt) - cnt) == 0));
65                 else
66                     assert ((($past(cnt) - cnt) == 9));
67             end
68         end
69     end
70 end
71 endmodule
72
```

RTL modeling in Verilog

In this task, we finally **implement** our counter using Verilog.

Using Verilog comes with various benefits: First, Verilog is natively supported by Yosys, which means that we may use the open-source version, rather than the (partly proprietary) Tabby CAD suite which comes with VHDL and SystemVerilog support. In case we use the open-source version of Yosys, we must include the assertions into the same Verilog file in which we implement our counter, because the open-source version of does not understand the SystemVerilog *bind* operator. This is what we do in Listing 2. While it is perfectly fine to keep the assertions in a separate file *tb_counter.sv*, we show in Listing 2 how to make use of *SymbiYosys* when using the open-source version of Yosys.

Listing 2 shows a skeleton Verilog file where we first add our (existing) properties. Now, our task is to create a behavioral model of our counter in Verilog. Extend the code that is given in Listing 2. Remember, in behavioral modeling, we specify the algorithmic behavior of our system, rather than designing the boolean network and connecting its inputs and outputs. In other words, we use arithmetic operators (such as '+', '-', etc.) to implement the counter.

We do not use multipliers in our design. Multipliers are expensive in terms of area, so we carefully check whether we may model the counter's behavior without them.

Listing 2: Counter in Verilog (*counter.v*)

```
1 module counter (clk, rst, mode, cnt);
2
3     // TODO: Put your behavioral code here
4
5
6
7     // Let's specify the counter's intended behavior here
8     `ifdef FORMAL
9         reg init = 1;
10        always @(posedge clk) begin
11            if (init) assume(rst);
12            else assume(!rst);
13            init <= 0;
14        end
15
16        always @(posedge clk) begin
17
18            if (rst) begin
19                assert (cnt == -10'sd50);
20            end
21
22            if (!rst) begin
23
24                //
25                // Check if counter value is never lower than MIN, larger than MAX, or
26                // equal to INV
27                //
28                assert (cnt <= 10'sd235);
29                assert (cnt >= -10'sd230);
30                assert (cnt != -10'sd11);
31
32                //
33                // Check if the counter value is correctly incremented and decremented
34                //
35
36                // Counting up
37                if ($past(mode)) begin
38                    if (!$past(rst)) begin
39                        if ($past(cnt) == -10'sd16) // INV - INC, counter jumped over INV
40                            assert ((cnt - $past(cnt)) == 10'sd10);
41                        else if ($past(cnt) <= 10'sd235 && $past(cnt) > 10'sd230) // cnt was near MAX
42                            assert ((cnt - $past(cnt)) == 10'sd0);
43                        else
44                            assert ((cnt - $past(cnt)) == 10'sd5);
45                    end
46                end
47
48                // Counting down
49                if (!$past(mode)) begin
50                    if (!$past(rst)) begin
51                        if ($past(cnt) == -10'sd2) // INV + DEC, counter jumped over INV
52                            assert ((($past(cnt) - cnt) == 10'sd18);
53                        else if ($past(cnt) >= -10'sd230 && $past(cnt) < -10'sd221) // cnt was near MIN
54                            assert ((($past(cnt) - cnt) == 10'sd0);
55                        else
56                            assert ((($past(cnt) - cnt) == 10'sd9);
57                    end
58                end
59            end
60        end
61    `endif
62 endmodule
63
```

We use the properties of the previous task to verify that we implement the counter's behavior as specified. Verilog is not strictly typed, which may lead to undesired side effects. By default, Verilog assumes a bit width of 32 bits for signals and constants. To be sure everything works as expected, we explicitly specify the number format for every constant in Listing 2, which apparently is 10-bit signed decimal.

To check our counter's correctness, we run SymbiYosys as given in Listing 3, along with the configuration file as given in Listing 4

Listing 3: Command line to verify our counter

```
1 sby -f counter.sby
```

Listing 4: Configuration file for SymbiYosys (*counter.sby*)

```
1 [options]
2 mode prove
3 expect pass
4
5 [engines]
6 aiger suprove
7
8 [script]
9 read_verilog -sv -formal counter.v
10 prep -top counter
11
12 [files]
13 counter.v
```

RTL synthesis

Once our counter's implementation conforms to its specification, it is time to synthesize our [register transfer level \(RTL\)](#) description into a netlist. We use Yosys to create the high-level netlist (in particular, the [RTL](#) netlist).

Listing 5 shows a basic synthesis script to perform behavioral synthesis with Yosys. In Line 1, the Verilog description of our counter is parsed into Yosys's intermediate representation. In Line 2, the hierarchy of the counter's design is elaborated. The *hierarchy* command looks which modules are instantiated by which other modules, and creates a hierarchy tree. The *-auto-top* option identifies the top-level entity, which in our case is the only module in the design: the *counter* module. The *proc* command given in In Line 3 synthesizes the design's processes (defined in *always* blocks). The *clean* command given in Line 4 removes unused cells and wires.

We may interactively issue all the commands from Listing 5 into the Yosys shell step-by-step, and quickly have a look at the resulting netlist by using the *show* command. Let's try it out! We start Yosys by typing *yosys* (all lower-case) into the command line.

Listing 5: Yosys script to synthesize our counter (*synth.ys*)

```
1 read_verilog counter.v
2 hierarchy -check -auto-top
3 proc
4 clean
```

Besides providing the interactive shell, Yosys also supports a batch mode. We simply enter the command given in Listing 6 to execute the Yosys script given in Listing 5.

Listing 6: Command to invoke (*synth.ys*) in batch mode

```
1 yosys -s synth.ys
```

Resource analysis

Now, let us have a look at the resources which are consumed by your counter, by adding the *stat* command to the script given in Listing 5. *stat*'s output may look like the output given in Listing 7. It basically shows the types and numbers of instantiated cells in the synthesized netlist, as well as wires to connect these cells. It may be interesting that the output in Listing 7 shows two instantiations of an adder cell in Line 13, as well as two instantiations of an subtractor cell in Line 18. Let's take some time to think about this; why may there be two adders, why two subtractors?

Listing 7: Example output of the *stat* command

```
1 7. Printing statistics.
2
3 === counter ===
4
5   Number of wires: 24
```

```

6 | Number of wire bits: 143
7 | Number of public wires: 4
8 | Number of public wire bits: 13
9 | Number of memories: 0
10 | Number of memory bits: 0
11 | Number of processes: 0
12 | Number of cells: 19
13 |   $add 2
14 |   $dff 1
15 |   $le 4
16 |   $mux 8
17 |   $ne 2
18 |   $sub 2

```

Coding style matters – Your task

To answer the above question, we primarily may focus on getting a correctly working implementation, without having any resource optimization in mind. In the general case, we may have two additions, and two subtractions because we most-likely implement one process in which the counter register is updated based on it's value in the previous clock cycle. This is perfectly okay for this simple use case; however, resource consumption is directly correlated with the coding style we use for our implementation.

To demonstrate this issue, our task is to implement the counter in Verilog with **just one adder**, and **zero subtractors**. Hint: have a look into what happens when we separate combinational logic from sequential logic.

We synthesize our design with Yosys as given in Listing 5 and use *stat* and *show* to investigate our design. *stat* should output something similar to Listing 8. As we can see, there is only one adder used in this design, and no subtractor.

Listing 8: Resources consumed by our Verilog counter

```

1 | Number of wires: 14
2 | Number of wire bits: 95
3 | Number of public wires: 5
4 | Number of public wire bits: 23
5 | Number of memories: 0
6 | Number of memory bits: 0
7 | Number of processes: 0
8 | Number of cells: 11
9 |   $add 1
10 |   $ge 2
11 |   $le 2
12 |   $mux 3
13 |   $ne 2
14 |   $sdff 1

```

This is a remarkable result: By optimizing our coding style only, we may control how many resources are instantiated in the RTL netlist. Even in this simple example, we reduced the number of adders/subtractors from (potentially) four to one. While this might not seem critical for this simple example, it however can have huge impact in real-world designs. Please remember: Always create clean and simple code in order to enable code optimization.

Submission details

Attach your extended *counter.v* to your submission e-mail.